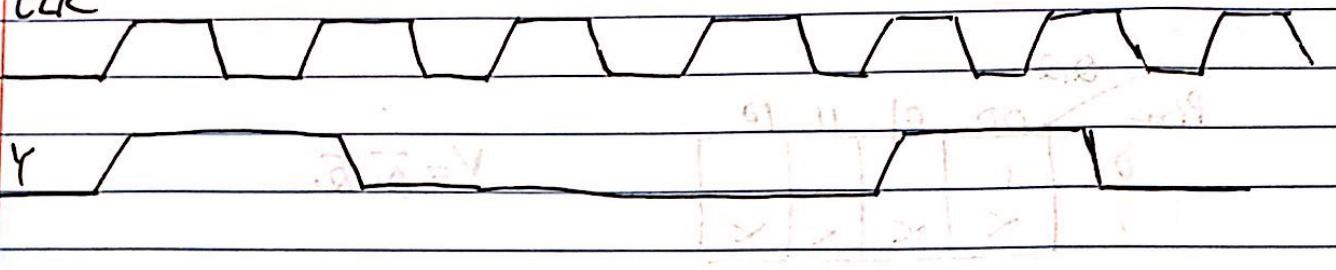


CS4341

Assignment 4

(1A)


CLK



(1B)

FSM


Reset

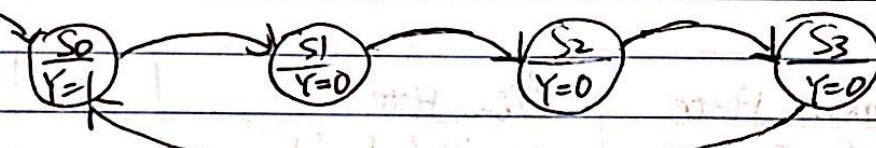

(1C)

Rest	Current State	Next State	Output
Q1 Q0	Q1 Q0	Q1+ Q0+	Y
1 0	X X	0 0	1
0 (S0)	0 0	0 1	1
0 (S1)	0 1	1 0	0
0 (S2)	1 0	1 1	0
0 (S3)	1 1	0 0	0

Q1+

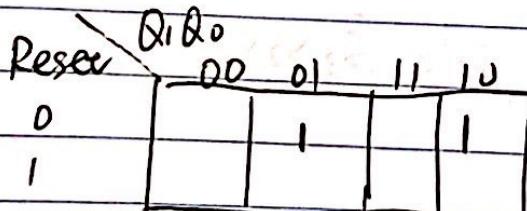

$$\begin{aligned} Q_1^+ &= \overline{\text{Rest}} \bar{Q}_1 Q_0 + \overline{\text{Reset}} Q_1 \bar{Q}_0 \\ &= \overline{\text{Reset}} (Q_1 \oplus Q_0) \end{aligned}$$

(2)

Rest	$Q_1 Q_0$	00	01	11	10
0	1	(1)			(1)
1					

$$Q_0^f = \overline{R_{ext}} + \overline{Q_0}$$

Rest	$Q_1 Q_0$	00	01	11	10
0	1	1			
1		x	x	x	x

$$Y = \overline{Q_1} \overline{Q_0}$$

Circuit on other file

(1D)	Rest	Current State	Next state	Y
		$S_3 \ S_2 \ S_1 \ S_0$	$S_3' \ S_2' \ S_1' \ S_0'$	
1	x	x x x x	0 0 0 0	1
$D(S_0)$	0 0	0 1	0 0 1 0	1
$D(S_1)$	0 0	1 0	0 1 0 0	0
$D(S_2)$	0 1	0 0	1 0 0 2 0	0
$D(S_3)$	1 0	0 0	0 0 0 1	0

 S_3'

Rest	$S_3 \ S_2 \ S_1 \ S_0$	00	01	10	010	100	1000
0	1				(1)		
1							

$$S_3' = \overline{S_3} \overline{S_2} \overline{S_1} \overline{S_0}$$

 S_2'

Rest	$S_3 \ S_2 \ S_1 \ S_0$	0001	0010	0100	1000
0	1			(1)	
1					

$$S_2' = \overline{S_3} \overline{S_2} \overline{S_1} \overline{S_0}$$

= ?

CS4341

Assignment

IS

(2A) State table

Present state	next state
A B C	A' B' C'
0 0 1	0 1 1
0 1 0	0 1 0
1 1 0	1 1 0
1 1 1	1 0 1
1 0 1	0 0 1

$$\bar{S}A = Sb$$

Excitation table for JK-Flip Flop.

Q Q'	J K
0 0	0 X
0 1	1 X
1 0	X 1
1 1	X 0

State excitation table

Present state	Next state	Input
A B C	A' B' C'	J1 k1 J2 k2 J3 k3
0 0 1	0 1 1	D X I X X b
0 1 1	0 1 0	D X X 0 X 1
0 1 0	1 1 0	I X X 0 O X
1 1 0	1 1 1	X 0 X 0 I X
1 1 1	1 0 1	X 0 X 1 X 0
1 0 1	0 0 1	X 1 O X X 0

11

18

14

(2B) k-map

		$A \backslash BC$	00	01	11	10
		0			1	
		1	X	X	X	

$$J_1 = BC$$

		$A \backslash BC$	00	01	11	10
		0		X	X	
		1	1			

$$K_1 = \bar{B}C$$

		$A \backslash BC$	00	01	11	10
		0		1	X	X
		1	X	X	X	

$$J_2 = \bar{A}C$$

		$A \backslash BC$	00	01	11	10
		0		X		
		1	X	X	1	

$$k_2 = Ac$$

		$A \backslash BC$	00	01	11	10
		0		X	X	
		1	X	X	X	

$$J_3 = AB$$

		$A \backslash BC$	00	01	11	10
		0			X	1
		1			X	

$$K_3 = \bar{A}B$$

(2C)

drawing on another file.

